

75 MARKS

$$\begin{array}{r} 2013 \\ 10884843 \\ \hline 5 \end{array}$$

- The pull-up network must be able to attain V_{DD} when necessary and the pull-down network must be the opposite of the pull-up network and must get V_G when necessary.

The PUN is also made up of PMOS transistors while the PDN is made up of NMOS transistors.

- The problem is the loss of precision in the lower-end bits.

- High-impedance is a state in a wire usually represented as Z and it is important because it doesn't matter if the output is a 1 or a 0 and it helps solve the fan-out problem.

- One use is to determine which inputs should go on in a circuit depending on what the control signals are set at.

Another use is to determine what value to return from a look-up table.

5. (10 marks) Given the following table of inputs versus outputs for a logic circuit, answer the following questions using variables of the form IN_x and OUT_x to denote the x^{th} bit and where $x = 0$ represents the lowest order bit.

Input	0	1	3	2	6	7	5	4
Output	0	1	2	4	4	2	1	0

- a) Draw the Karnaugh Maps for each output bit, clearly identifying the inputs and outputs.
b) Minimize each K-Map using SOP form and clearly identify your solution. **Please do not attempt to optimize your solution beyond the K-Map derivation!**

IN_2	IN_1	IN_0	OUT_2	OUT_1	OUT_0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	1	0	0
1	1	1	0	1	0

a) OUT_2

IN_2	IN_1	IN_0	
	00	01	11 10
0			1
1			1

OUT1

IN2	IN1 IN0	00	01	11	10
0				1	
1				1	

OUT_0

IN_2	IN_1	IN_0
0	00	01
1		

b) $OUT_2 = \overline{IN_1} \overline{IN_0}$

$OUT_1 = IN_1 IN_0$

$OUT_0 = \overline{IN_1} IN_0$

10

6. (10 marks) Write the Entity and Architecture VHDL code for the logic function

$$F(x_2, x_1, x_0) = \Sigma m(1, 2, 4, 7)$$

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY testquestion IS
```

```
    PORT (x2, x1, x0 : IN BIT ;  
          F          : OUT BIT);
```

```
END testquestion
```

```
ARCHITECTURE LogicFunc OF testquestion IS
```

```
BEGIN
```

```
    F <= (x2 AND NOT x1) AND NOT x0 OR (NOT x2 AND NOT x1 AND x0) OR  
         (x2 AND x1 AND x0) OR (NOT x2 AND x1 AND NOT x0);
```

```
END LogicFunc;
```

8

7. (8 marks) Express the following K-maps as logic functions of the required form.

a) $F(x_4, x_3, x_2, x_1) = \overline{x_3} \overline{x_2} \overline{x_1} + x_4 \overline{x_3} \overline{x_1} + x_3 \overline{x_2} x_1 + x_4 x_3 x_1 + \overline{x_4} x_3 x_2 \overline{x_1}$ Sum of Products Form

F

		x ₂ x ₁			
		00	01	11	10
x ₄ x ₃	00	1	0	0	0
	01	0	1	0	1
	11	0	1	1	0
	10	1	0	0	1

b) $G(x_1, x_2, x_3, x_4) = (x_2 + x_4)(x_1 + \overline{x_2})(\overline{x_2} + \overline{x_4})$ Product of Sums Form

G

		x ₃ x ₄			
		00	01	11	10
x ₁ x ₂	00	0	1	1	0
	01	0	0	0	0
	11	1	0	0	1
	10	0	1	1	0

8. (4 marks) What is the difference between a binary encoder and a binary decoder?

A binary decoder has n inputs and produces 2^n outputs which are one-hot encoded or only one of the outputs is 1. A binary encoder has 2^n inputs which are one-hot encoded and produces n outputs.

9. (8 marks) Given the following VHDL code, draw the timing diagram for the resulting circuit as if you were the Max+plus II development environment.


```

LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY midterm IS
    PORT (
        w1, w0, s : IN  STD_LOGIC;
        f         : OUT STD_LOGIC);
END midterm;

ARCHITECTURE behavior OF midterm IS
BEGIN
    WITH s SELECT
        f <= (w1 AND w0) WHEN '0'
            (w1 OR w0) WHEN OTHERS;
END behavior;

```

 

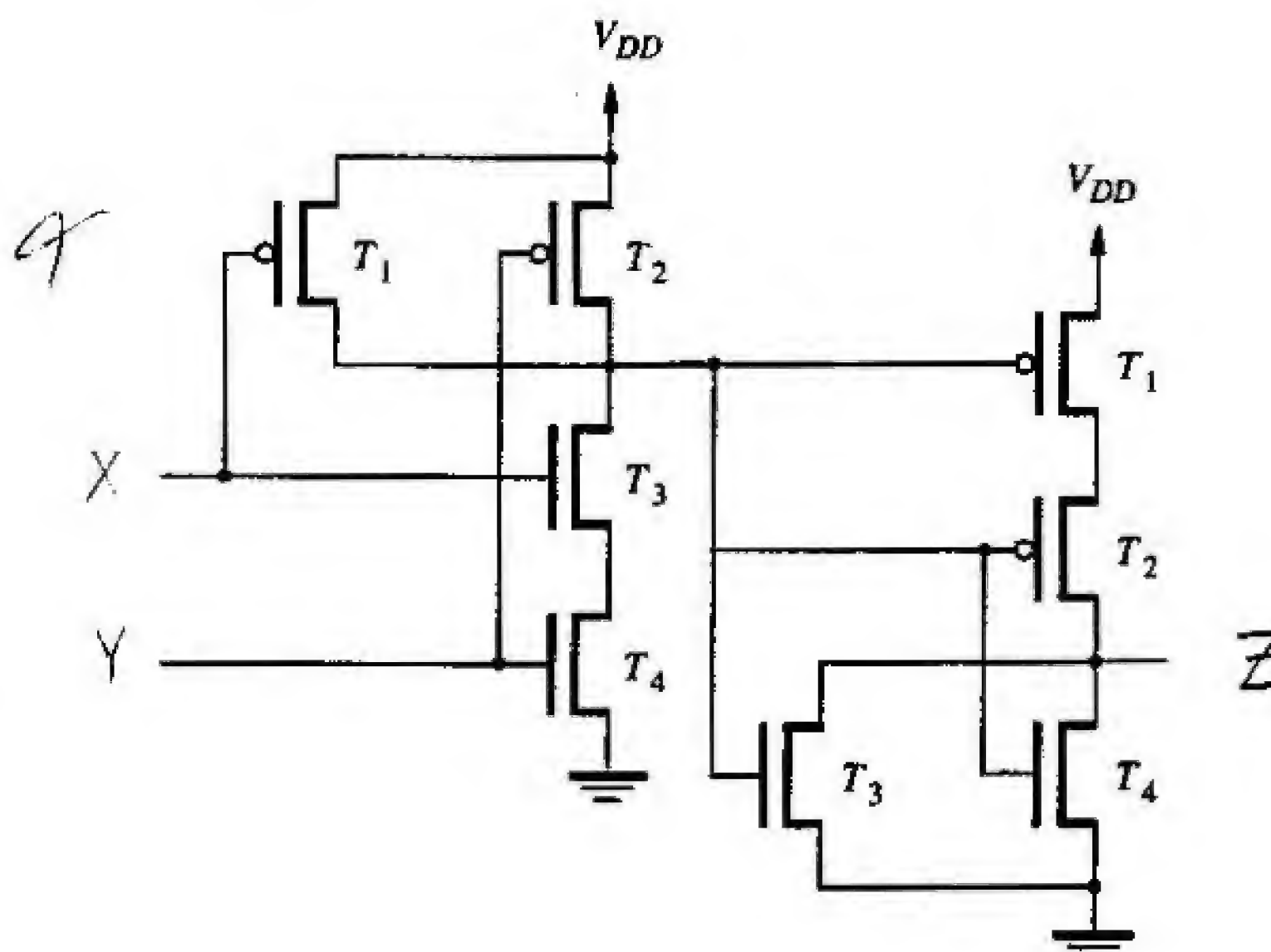10. (4 marks) Express the logic function implemented by the following CMOS circuit in Sum Of Products form.



AND function

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

z	y	
x	0	1
	0	1
1	0	1

$$Z = xy$$

11. (9 marks) Analyze the following timing diagram to determine the logic function that it represents. Clearly state the logic function and design a circuit that implements the logic function using NAND gates only.



b1	b0	a1	a0
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	1

XNOR OR

a1 = EXCLUSIVE NOR

a0 = OR

Name:	20.0ns	40.0ns	60.0ns	80.0ns
[I] b1	0	1	1	1
[I] b0	0	0	1	1
[O] a1	1	0	0	1
[O] a0	0	1	1	1

  

3

12. (6 marks) What is the distinguishing characteristic for each of combinational, sequential, and synchronous systems.

A sequential system is a system where one thing is done and the next thing starts as soon as the first thing finishes.

A combinational system is one where some parts can be done at the same time to speed up the system.

A synchronous system is where everything is done at the same time.